




Mark _____ / 33

1. Name the following electrical circuit components.

- a  power source / battery
- b  open switch = 1 each
- c  light globe (3)

2. Draw the symbols for the following electrical components.

- (a) closed switch  (3)
- (b) resistor  (3)
- (c) ammeter  = 1 each

3. Write the unit and unit symbol used to measure:


- | | Unit | Symbol | |
|--------------|----------------|----------------------------|-----|
| a current | <u>amperes</u> | <u>A / mA</u> | (1) |
| b voltage | <u>volts</u> | <u>V</u> | (1) |
| c resistance | <u>ohms</u> | <u>Ω</u> | (1) |
- (3)

4. Define each the following sets of light globes as in either series or in parallel circuit.

- a  parallel circuit = 1 (2)
- b  Series circuit = 1 (2)


5. Calculate the supply voltage of the battery arrangement for each set of torch batteries.

5a.

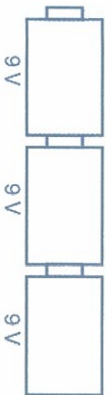

Supply Voltage 27 V = 1mk


5b.

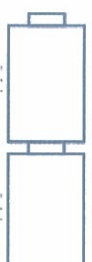

supply voltage 3 V = 1mk.

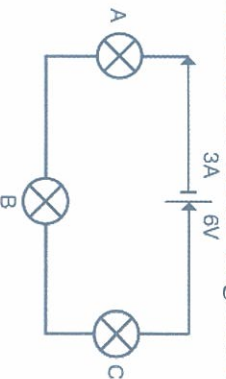(2)

Look at the circuit diagram to answer Q 6, Q 7 & Q8



6. All globes in the circuit above were working correctly when globe A broke and stopped glowing. Which of the globes would also have stopped glowing because of this?

- ☒ A all globes
☐ B only globe C

- ☐ C only globe B
☐ D no other globes stop glowing

(1)

7. Globe A was then replaced so that all globes in the circuit above were once again working. Soon after, globe C broke and stopped glowing. Which of the other globes would also stop glowing because of this?

- ☒ A all globes
☐ B only globe C

- ☐ C only globe A
☐ D only globe B


(1)
 (1)

8. The circuit is set up as a Series circuit.

(1)
 (1)

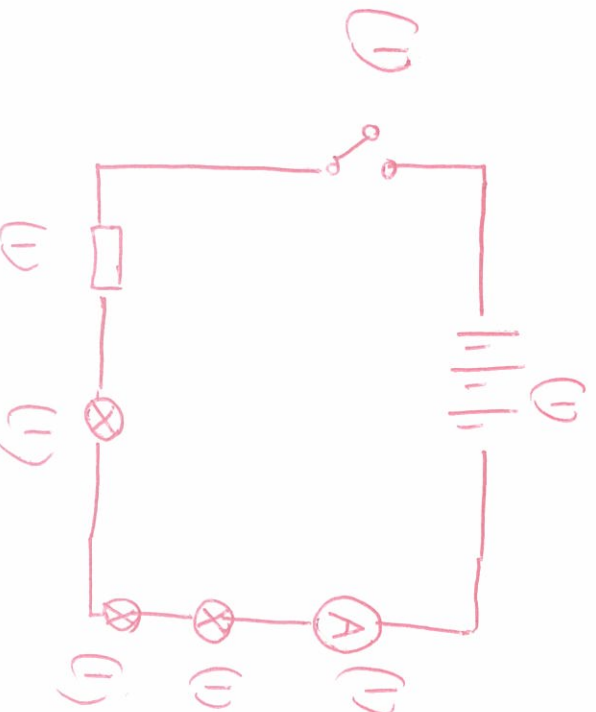9. In the space below : Draw a circuit diagram


a battery of 3 cells, a switch, an ammeter, a single resistor, and 3 globes in series to each other
 (Hint: Use ruler & pencil, cross off each label as you use it!)



(7)

10. Write the voltage over each of the light globes in the circuits below.


a

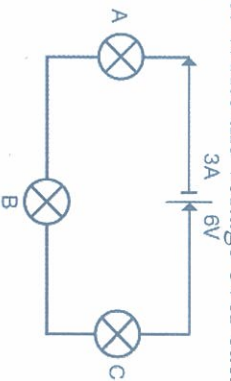

Globe A 2V
Globe B 2V
Globe C 2V

(3)


b

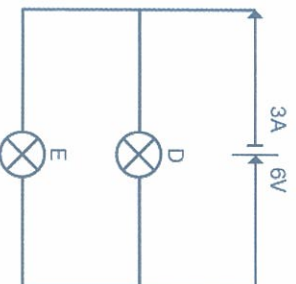

Globe D 6V
Globe E 6V

(2)

c

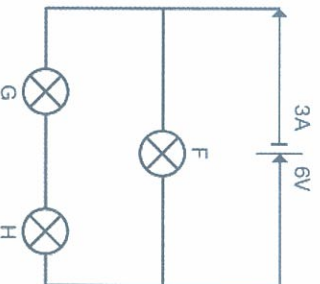


Globe F 6V
Globe G 3V
Globe H 3V

(3)

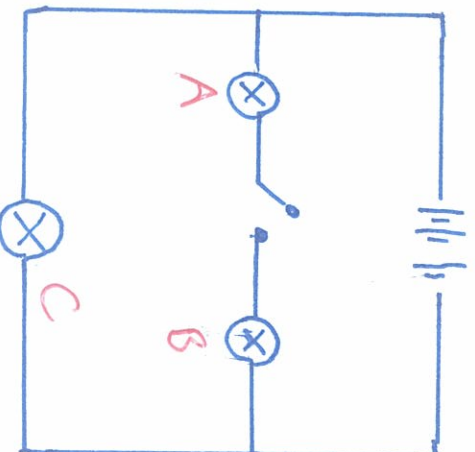11. Look at this circuit

Describe what will occur when the switch is closed / and switch open



Switch closed: All globes will light up (1)

Switch open: Only globe C will light up (1) (2)