

Mark \_\_\_\_\_ / 33

1. **Name** the following electrical circuit components.

a



\_\_\_\_\_

b



\_\_\_\_\_

c



\_\_\_\_\_

(3)

2. Draw the symbols for the following electrical components.

(a) closed switch



(b) resistor



(c) ammeter



(3)

3. **Write** the unit and unit symbol used to measure:

Unit

Symbol

a current

\_\_\_\_\_

\_\_\_\_\_

b voltage

\_\_\_\_\_

\_\_\_\_\_

c resistance


\_\_\_\_\_

\_\_\_\_\_

(3)


4. **Define** each the following sets of light globes as in either series or in parallel circuit.

a

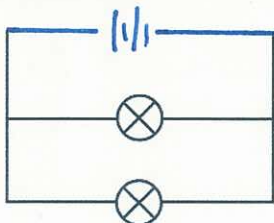

\_\_\_\_\_

b

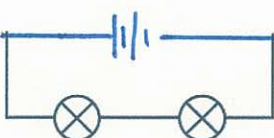

\_\_\_\_\_

(2)


5. Calculate the supply voltage of the battery arrangement for each set of torch batteries.

5a.



Supply Voltage \_\_\_\_\_


5b.

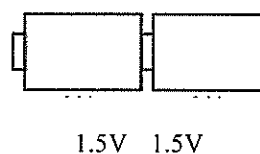

supply voltage \_\_\_\_\_

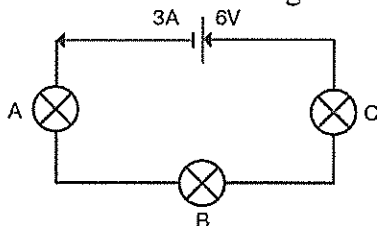(2)

Look at the circuit diagram to answer Q 6, Q 7 & Q8



6. All globes in the circuit above were working correctly when globe A broke and stopped glowing. Which of the globes would also have stopped glowing because of this?

- A all globes
- B only globe C
- C only globe B
- D no other globes stop glowing

(1)

7. Globe A was then replaced so that all globes in the circuit above were once again working. Soon after, globe C broke and stopped glowing. Which of the other globes would also stop glowing because of this?

- A all globes
- B only globe C
- C only globe A
- D only globe B

(1)

8. The circuit is set up as a \_\_\_\_\_ circuit.

(1)


9. In the space below : Draw a circuit diagram

**a battery of 3 cells, a switch, an ammeter, a single resistor, and 3 globes in series to each other**

(Hint: Use ruler & pencil, cross off each label as you use it!)

(7)

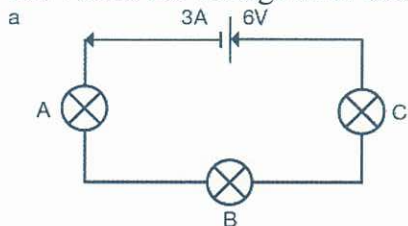10. Write the voltage over each of the light globes in the circuits below.




Globe A \_\_\_\_\_

Globe B \_\_\_\_\_

Globe C \_\_\_\_\_


(3)

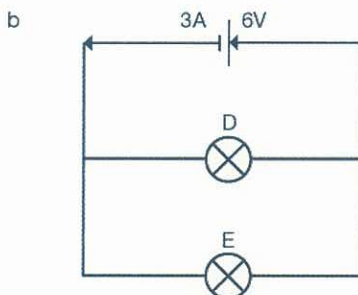

Globe D \_\_\_\_\_

Globe E \_\_\_\_\_

(2)

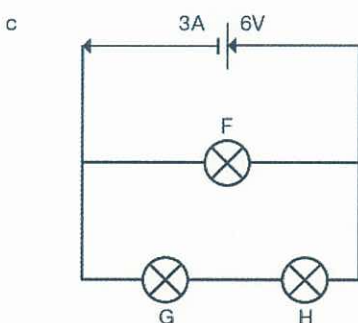

Globe F \_\_\_\_\_


Globe G \_\_\_\_\_

Globe H \_\_\_\_\_

(3)

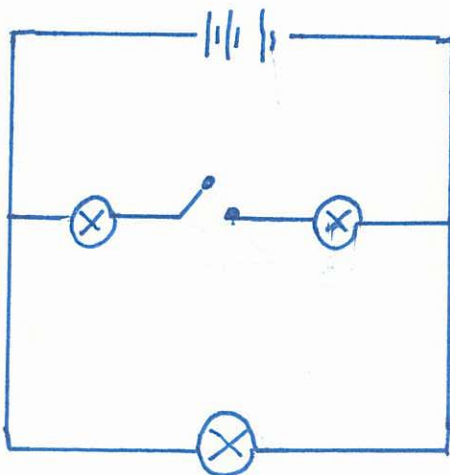11. Look at this circuit

Describe what will occur when the switch is closed / and switch open



Switch closed:

Switch open:

(2)