
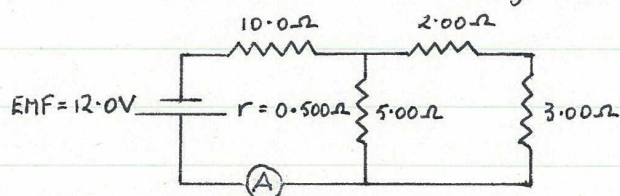


1. A wire has a resistance of  $20.0\ \Omega$ . If the wire is drawn out to three times its original length and its diameter is halved, what is its new resistance? (3)

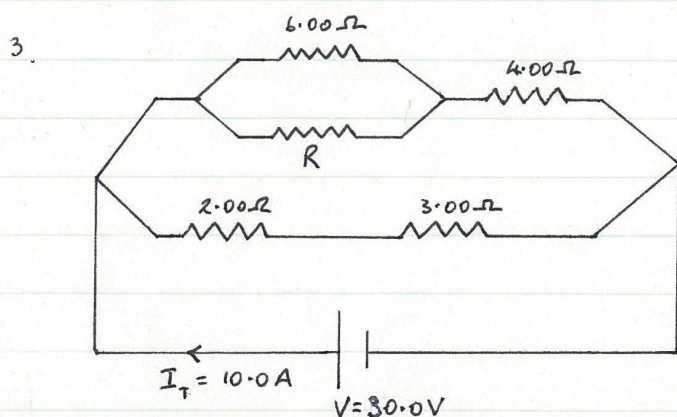2. From the circuit diagram shown, calculate:



- (a) the total resistance,  
(b) the current that flows.  
(c) the terminal voltage. (5)



Given the total current in the circuit at left is  $10.0\text{ A}$ , calculate:

- (a) the current in the  $2.00\ \Omega$  resistor,  
(b) the potential drop across the  $4.00\ \Omega$  resistor  
(c) the value of the resistance  $R$ . (5).

4. An electric kettle has a heating element of resistance  $24.0\ \Omega$  and operates at  $10.0\text{ A}$  at  $2.40 \times 10^2\text{ V}$ . It is used to heat  $0.900\text{ kg}$  of water from  $20.0^\circ\text{C}$  to boiling point. Given the kettle is made out of  $0.450\text{ kg}$  stainless steel (specific heat  $= 7.20 \times 10^2\text{ J kg}^{-1}\text{ K}^{-1}$ ), and  $10.0\%$  of the heat energy supplied is lost to the atmosphere, calculate the time taken for the kettle to boil.

$$(c_{\text{water}} = 4.18 \times 10^3\text{ J kg}^{-1}\text{ K}^{-1}, \quad L_{\text{vapourisation (water)}} = 2.25 \times 10^6\text{ J kg}^{-1}). \quad (5)$$

5. Define the following terms:

- (a) current  
(b) potential difference. (2)

6. Draw a diagram to show how five  $3.00\ \Omega$  resistors can be joined to give an overall resistance of  $7.00\ \Omega$ . (2)